

## HOMEWORK for TUESDAY, JULY 5, 2005

Determine the currents in the following circuits, and construct the  $R - I - \Delta V - P$  table for each circuit. Check that the powers are correct. Also, determine the electric potentials at the points marked.

